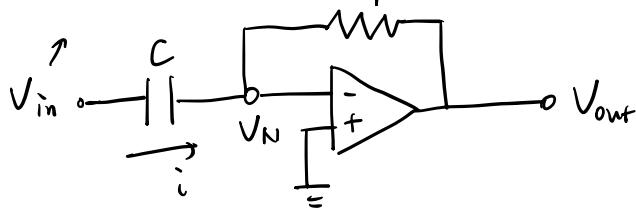


## # Theoretical Basis

### ① Rate (Derivative) Circuit



1) For the capacitor,

$$(V_{in} - V_N) \cdot C = \dot{q}$$

Take the derivative of both sides.

$$(\dot{V}_{in} - \dot{V}_N) \cdot C = \dot{\dot{q}}$$


$$\text{Since } V_N \equiv 0 \Rightarrow \dot{V}_N = 0$$

$$\Rightarrow \dot{V}_{in} C = \dot{\dot{q}} = i$$

2) For the operational amplifier,

$$\frac{V_N - V_{out}}{R} = i \Rightarrow V_{out} = -iR = -(RC)\dot{V}_{in}$$


To determine the direction of  $i$

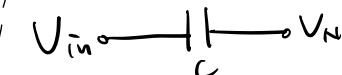


Suppose  $\dot{V}_{in} > 0$ , which means that

the value of  $V_{in}$  is increasing.

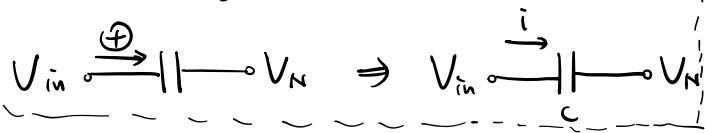$\Rightarrow$  There will be more positive charges on the right-side of the capacitor.



### ② Area (Integral) Circuit

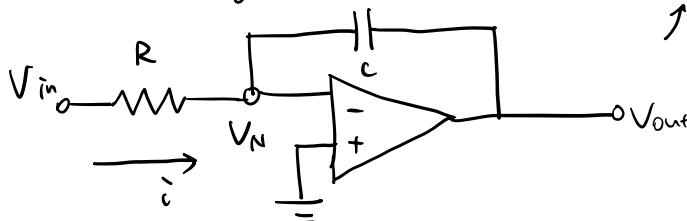

① For the resistor R on the input terminal,

$$\frac{V_{in} - V_N}{R} = i \xrightarrow{V_N = 0} i = \frac{V_{in}}{R}$$

② For the operational amplifier,

$$(V_N - V_{out}) \cdot C = \dot{q} \xrightarrow{V_N = 0} \dot{q} = -V_{out} \cdot C$$

Take the derivatives of both sides,

$$\dot{\dot{q}} = -C \cdot \dot{V}_{out} \Rightarrow \dot{V}_{out} = -\frac{1}{C} \cdot \frac{V_{in}}{R} = -\frac{1}{RC} \cdot V_{in}$$

Take the Integrals of both sides,


$$V_{out} = -\frac{1}{RC} \int V_{in} dt$$

★ Key points:

the topology position of resistor and capacitor in the rate/area circuits.


## # Experiment 5 : Performing Rate and Area Operations

Review . Buffer circuit

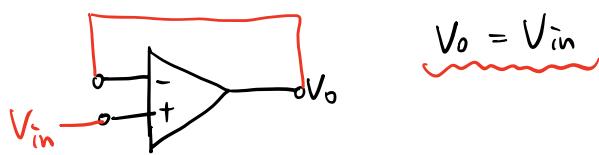

Hint .

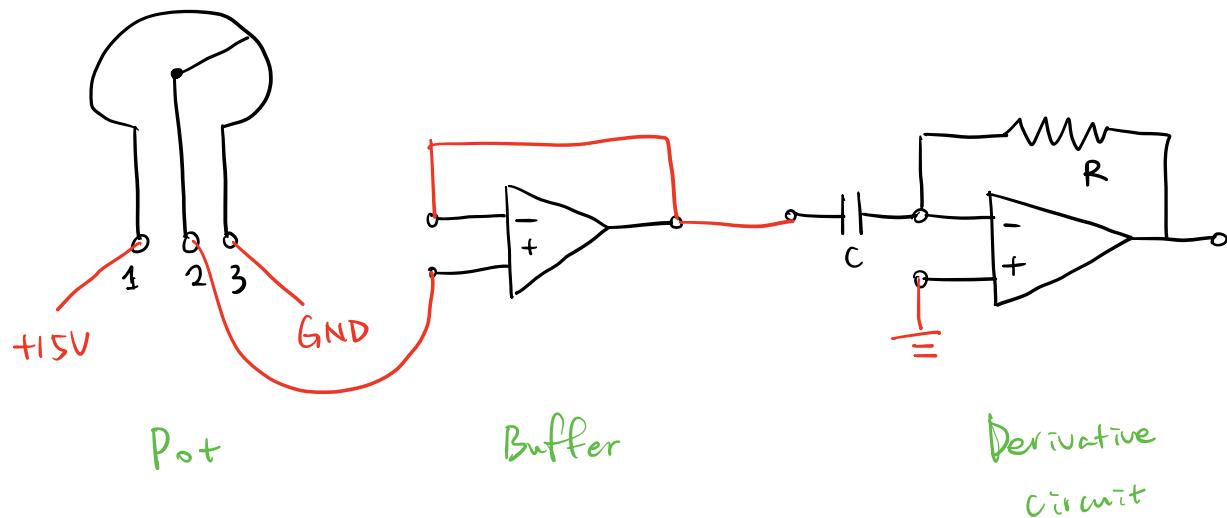- ① Connection diagram of the derivative circuit



Safety . A resistor can be connected before the pot.

Deliverables :

- ① Pics of derivative and integral circuits
- ② Group Number + Name